

# Analog IC Design: Assignment-2

Spring 2026, IIIT Hyderabad

Name: **Chamarthy Madhan Sai Krishna** Roll No: **2023102030**

Due Date: February 23, 2026 (18:00 hrs)

## Question 1: n-channel MOSFET Characteristics

Considering  $V_{DS} = 1V$  and  $\frac{W}{L} = \frac{500n}{180n}$ :

(a)  $I_D$  vs  $V_{GS}$  and  $g_m$  vs  $V_{GS}$  Plots

Cases: (i)  $V_{SB} = 0V$ , (ii)  $V_{SB} = 0.9V$ , (iii)  $V_{SB} = -0.9V$ .

### Schematic and Simulation Setup

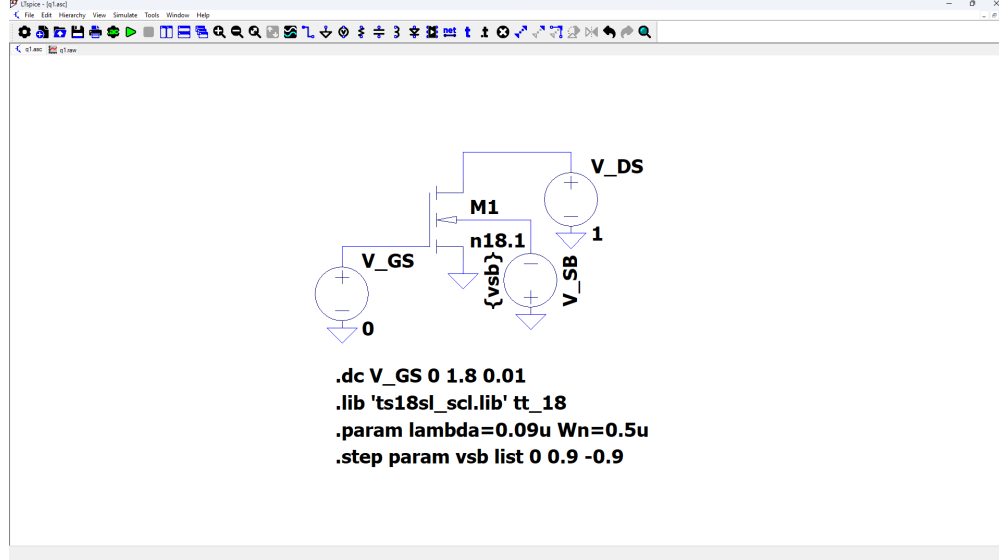


Figure 1: Schematic for  $I_D$  vs  $V_{GS}$  and  $g_m$  vs  $V_{GS}$  simulations.

(b) Reference Current  $I_{D0}$

For  $V_{SB} = 0V$  and  $V_{GS} = 0.9V$ :

- $I_{D0} = 50.576\mu A$
- $g_{m0} = 174.914\mu S$

 


Figure 2:  $I_{D0}$  value at  $V_{GS} = 0.9V$  and  $V_{SB} = 0V$ .

 


Figure 3:  $g_{m0}$  value at  $V_{GS} = 0.9V$  and  $V_{SB} = 0V$ .

(c)  $g_m$  variations for  $V_{GS} = 0.9V$

- Case  $V_{SB} = 0.9V$ :  
 $V_{SB} = 0.9V$ :  $I_D = 31.1079\mu A$ ,  $g_m = 169.21\mu S$   
 $V_{SB} = -0.9V$ :  $I_D = 60.6638\mu A$ ,  $g_m = 198.199\mu S$   
 $V_{SB} = 0V$ :  $I_D = 50.576\mu A$ ,  $g_m = 194.914\mu S$   
Variation when  $V_{SB} = 0.9V = \frac{169.21 - 194.914}{194.914} \times 100\% = -13.65\%$   
Variation when  $V_{SB} = -0.9V = \frac{198.199 - 194.914}{194.914} \times 100\% = 1.68\%$
- Case  $V_{SB} = -0.9V$ :

 


Figure 4:  $g_m$  variation at  $V_{GS} = 0.9V$  for different  $V_{SB} = 0.9$ .

 


Figure 5:  $g_m$  variation at  $V_{GS} = 0.9V$  for different  $V_{SB} = -0.9$ .

(d)  $g_m$  Variation for  $I_D = I_{D0}$

- Case  $V_{SB} = 0.9V$ :  
 $V_{SB} = 0.9V$ :  $I_D = 50.5756\mu A$ ,  $g_m = 198.811\mu S$   
 $V_{SB} = -0.9V$ :  $I_D = 50.57562\mu A$ ,  $g_m = 185.627\mu S$   
 $V_{SB} = 0V$ :  $I_D = 50.576\mu A$ ,  $g_m = 194.914\mu S$   
Variation when  $V_{SB} = 0.9V = \frac{198.811 - 194.914}{194.914} \times 100\% = 2.00\%$   
Variation when  $V_{SB} = -0.9V = \frac{185.627 - 194.914}{194.914} \times 100\% = -4.76\%$
- Case  $V_{SB} = -0.9V$ :

 


Figure 6:  $g_m$  variation at  $I_D = I_{D0}$  for different  $V_{SB} = 0.9$ .

 


Figure 7:  $g_m$  variation at  $I_D = I_{D0}$  for different  $V_{SB} = -0.9$ .

## Simulation Results (Plots)

 


Figure 8: Simulated  $I_D$  vs  $V_{GS}$  for different  $V_{SB}$  values.

 


Figure 9: Simulated  $g_m$  vs  $V_{GS}$  for different  $V_{SB}$  values.

## Discussion

### 1. Physical Phenomenon: The Body Effect

The primary cause for the variations observed in the  $I_D$  and  $g_m$  plots is the **Body Effect**. In the 180 nm technology, the threshold voltage ( $V_T$ ) is dependent on the source-to-bulk voltage ( $V_{SB}$ ). As  $V_{SB}$  increases (e.g., to 0.9V), the depletion region width increases, which raises  $V_T$ . Conversely, a negative  $V_{SB}$  ( $-0.9V$ ) reduces the threshold voltage.

### 2. Case (c): Constant $V_{GS}$ Variation

In this voltage-biased configuration,  $V_{GS}$  is held constant at 0.9V. Because  $V_T$  increases with  $V_{SB}$ ,

the effective overdrive voltage ( $V_{GS} - V_T$ ) is reduced, leading to a significant drop in transconductance. Using  $V_{SB} = 0V$  as a reference ( $g_m = 194.914 \mu S$ ):

- **For  $V_{SB} = 0.9V$ :**  $g_m = 169.21 \mu S$ . This represents a variation of  $-13.19\%$ .
- **For  $V_{SB} = -0.9V$ :**  $g_m = 198.199 \mu S$ . This represents a variation of  $1.69\%$ .

### 3. Case (d): Constant $I_D$ Variation

In the current-biased configuration,  $I_D$  is held constant at approximately  $50.58 \mu A$ . Here,  $V_{GS}$  automatically adjusts to compensate for changes in  $V_T$ , which stabilizes the transconductance.

- **For  $V_{SB} = 0.9V$ :**  $g_m = 198.811 \mu S$ . This represents a variation of only  $2.00\%$ .
- **For  $V_{SB} = -0.9V$ :**  $g_m = 185.627 \mu S$ . This represents a variation of  $-4.76\%$ .

### 4. Core Inference

Comparing these cases reveals that **current-biasing (Part d) is significantly more robust** against substrate potential fluctuations than voltage-biasing (Part c). While the transconductance varied by over  $13\%$  in the voltage-biased case, it remained within approximately  $5\%$  when the current was fixed. This is a primary reason why analog designers prefer current-source biasing to ensure stable amplifier gain.

### 5. Analytical Match

The results align with the analytical square-law model where  $g_m = \sqrt{2\mu C_{ox} \frac{W}{L} I_D}$ . Under constant  $I_D$ , the  $g_m$  remains relatively stable to the first order. Small observed variations in simulation are attributed to second-order effects like mobility degradation and depletion capacitance changes inherent in the 180 nm process.

## Question 2: Transconductance Analysis

Using the circuit in Figure 1 with  $V_{DD} = 1.8V$ .

### (a) $g_m$ vs $I_D$ Curve

Sweep  $I_D$  from  $10\mu A$  to  $1mA$  for: 1.  $(W/L) = \frac{3\mu m}{1\mu m}$  2.  $(W/L) = \frac{0.45\mu m}{0.18\mu m}$

 


Figure 10: Schematic for  $g_m$  vs  $I_D$  simulation for  $(W/L) = 3u/1u$ .

 


Figure 11: Simulated  $g_m$  vs  $I_D$  for  $(W/L) = 0.45u/0.18u$ .

### 1. Comparison with Analytical Form

Between the two cases, the  $(W/L) = 3\mu m/1\mu m$  transistor exhibits a  $g_m$  plot that is significantly closer to the expected analytical form  $g_m = 2I_D/(V_{GS} - V_T)$ . This is primarily because the threshold

voltage ( $V_T$ ) used for the calculation was extracted for a  $1\mu\text{m}$  channel length in the previous assignment. Consequently, the analytical model remains well-calibrated for this specific device geometry.

## 2. Impact of Channel Length on $V_T$

The short-channel case ( $0.18\mu\text{m}$ ) deviates from the expected form because the threshold voltage is not constant across different channel lengths. Due to short-channel effects such as Drain-Induced Barrier Lowering (DIBL), the  $V_T$  for the  $0.18\mu\text{m}$  device differs from the  $1\mu\text{m}$  reference, leading to inaccuracies when applying the same analytical constants.

## 3. Velocity Saturation

Furthermore, long-channel devices like the  $1\mu\text{m}$  transistor better obey the square-law equations over a larger current range. In contrast, the  $0.18\mu\text{m}$  device experiences velocity saturation at higher values of  $I_D$ , causing the transconductance to level off or "saturate" earlier than predicted by the simple  $2I_D/V_{OV}$  model. This physical limitation further separates the short-channel performance from the theoretical ideal.

### (b) Max Transconductance and Saturation

- $g_{m,max}$  observed for  $(W/L) = 3u/1u$ :  $841.392 \mu\text{S}$
- $g_{m,max}$  observed for  $(W/L) = 0.45u/0.18u$ :  $443.218 \mu\text{S}$
- $I_D$  at which  $g_m$  saturates for  $(W/L) = 3u/1u$ :  $0.792 \text{ mA}$
- $I_D$  at which  $g_m$  saturates for  $(W/L) = 0.45u/0.18u$ :  $417.87 \mu\text{A}$
- $g_{m,use} = 0.8 \times g_{m,max} = 0.8 \times 841.392\mu\text{S} = 673.114\mu\text{S}$  for  $(W/L) = 3u/1u$
- $g_{m,use} = 0.8 \times g_{m,max} = 0.8 \times 443.218\mu\text{S} = 354.574\mu\text{S}$  for  $(W/L) = 0.45u/0.18u$
- $I_D$  for  $g_{m,use} = 0.8 \times g_{m,max}$  for  $(W/L) = 3u/1u$ :  $0.368 \text{ mA}$
- $I_D$  for  $g_{m,use} = 0.8 \times g_{m,max}$  for  $(W/L) = 0.45u/0.18u$ :  $0.119 \text{ mA}$

 


Figure 12:  $g_{m,max}$  for  $(W/L) = 3u/1u$ .



 


Figure 13:  $g_{m,max}$  for  $(W/L) = 0.45u/0.18u$ .

 


Figure 14: Saturation of  $g_m$  for  $(W/L) = 3u/1u$ .

 


Figure 15: Saturation of  $g_m$  for  $(W/L) = 0.45u/0.18u$ .

 


Figure 16: Determining  $I_D$  for  $g_{m,use} = 0.8 \times g_{m,max}$  for  $(W/L) = 3u/1u$ .

 


Figure 17: Determining  $I_D$  for  $g_{m,use} = 0.8 \times g_{m,max}$  for  $(W/L) = 0.45\mu/0.18\mu$ .

### (c) Scaling Parameters

#### 1. Scaling Methodology

For the short-channel device with  $(W/L) = 0.45\mu\text{m}/0.18\mu\text{m}$ , the design is scaled to obtain  $g_{m,req} = 4 \times g_{m,use}$  while preserving circuit speed. By keeping the channel length  $L$  fixed at 180 nm and scaling the width  $W$  and bias current  $I_D$  by a factor of 4, the transit frequency ( $f_T \propto g_m/C_{gg}$ ) remains constant.

#### 2. Calculated Parameters

Based on the values obtained in part (b), the parameters are scaled as follows:

For  $(W/L) = 0.45\mu\text{m}/0.18\mu\text{m}$ :

- **Target Transconductance:**  $g_{m,req} = 4 \times 354.574 \mu\text{S} = 1.418 \text{ mS}$
- **Scaled Width ( $W_{new}$ ):**  $4 \times 0.45 \mu\text{m} = 1.8 \mu\text{m}$
- **Scaled Bias Current ( $I_{D,new}$ ):**  $4 \times 0.119 \text{ mA} = 0.476 \text{ mA}$

For  $(W/L) = 3\mu\text{m}/1\mu\text{m}$ :

- **Required Transconductance:**  $g_{m,req} = 4 \times 673.114 \mu\text{S} = 2.692 \text{ mS}$
- **Scaled Width:**  $W_{new} = 4 \times 3 \mu\text{m} = 12 \mu\text{m}$
- **Scaled Bias Current:**  $I_{D,new} = 4 \times 0.368 \text{ mA} = 1.472 \text{ mA}$

#### 3. Simulation Results for $g_{m,req}$

For  $(W/L) = 3\mu\text{m}/1\mu\text{m}$ , the simulated  $g_m$  at  $I_D = 1.472 \text{ mA}$  is approximately  $2.615 \text{ mS}$ , confirming that the scaling approach successfully achieves the target transconductance while maintaining the same transit frequency. For  $(W/L) = 0.45\mu\text{m}/0.18\mu\text{m}$ , the simulated  $g_m$  at  $I_D = 0.476 \text{ mA}$  is approximately  $1.24 \text{ mS}$ , also confirming the effectiveness of the scaling method.

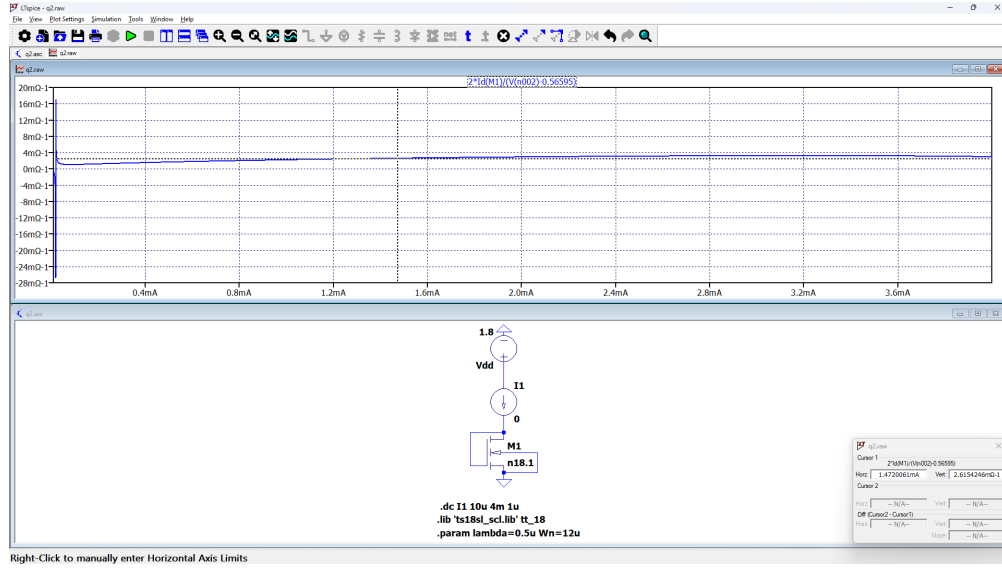


Figure 18: Scaling of  $g_m$  with  $I_D$  for  $(W/L) = 3u/1u$ .

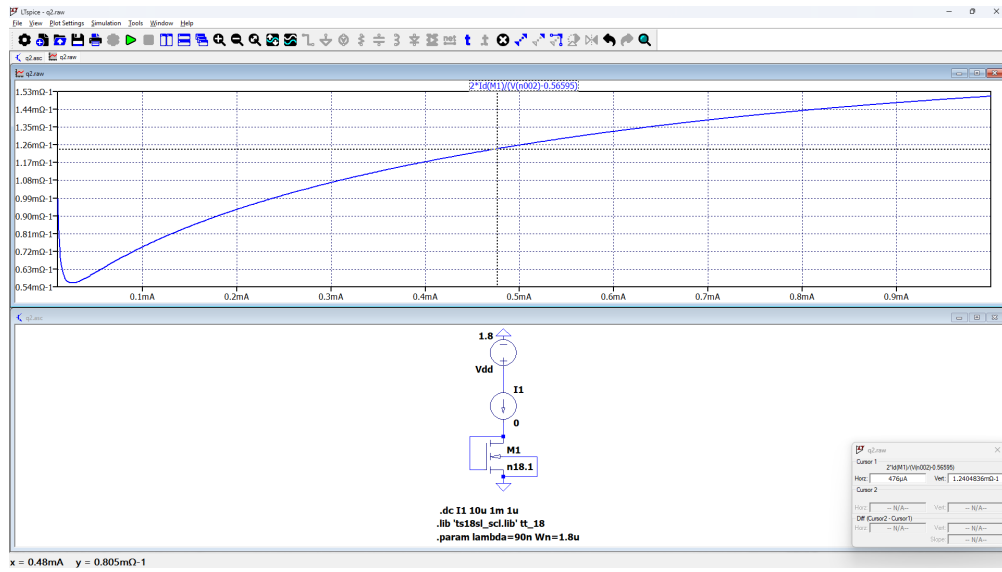


Figure 19: Scaling of  $g_m$  with  $I_D$  for  $(W/L) = 0.45u/0.18u$ .

### Question 3: CS Amplifier Design ( $g_m/I_D$ Approach)

Specifications:  $A_v > 60$ ,  $f_u = 100\text{MHz}$ ,  $C_L = 1\text{pF}$ ,  $V_{DD} = 1.8\text{V}$ ,  $V^* = \frac{2I_D}{g_m} = 200\text{mV}$ .

#### (a) Channel Length Selection

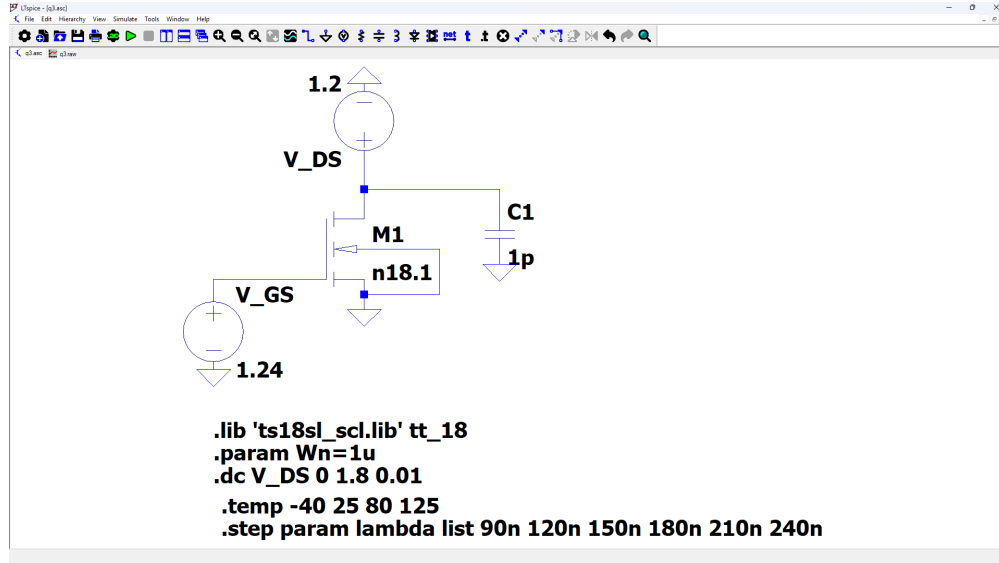


Figure 20: Schematic for  $g_m r_o$  vs  $V_{DS}$  simulation for different channel lengths.

 


Figure 21: Length parameter selection based on  $g_m r_o$  vs  $V_{DS}$  plots (Typical Corner; Sweep across channel lengths).

 


Figure 22: Output swing range determination based on  $g_m r_o$  vs  $V_{DS}$  plots for the chosen channel length.

**Chosen  $L$ :** 300 nm (300 nm) based on the best trade-off between gain and output swing.  
**Output Swing Range:** 1.8 - 1.11 V = 0.69 V

## (b) Process and Temperature Variations

 


Figure 23: Typical-Typical corner (TT)  $g_m r_o$  vs  $V_{DS}$  for the chosen channel length and Temperature sweep.

 


Figure 24: Slow-Slow corner (SS)  $g_m r_o$  vs  $V_{DS}$  for the chosen channel length and Temperature sweep.

 


Figure 25: Fast-Fast corner (FF)  $g_m r_o$  vs  $V_{DS}$  for the chosen channel length and Temperature sweep.

### (c) Design Calculations

 


Figure 26: Finding the bias point for  $g_m/I_D = 10$  for the chosen channel length.

 


Figure 27: Determining the unit width current at the bias point for  $g_m/I_D = 10$ .



 


Figure 28: Scaling the width to achieve the required current for the target  $g_m$ .

### 1. Required Transconductance and Current

To achieve the target unity-gain bandwidth  $f_u = 100$  MHz with a load capacitance  $C_L = 1$  pF, the required transconductance is:

$$g_m = 2\pi \cdot f_u \cdot C_L = 2\pi \cdot 100 \text{ MHz} \cdot 1 \text{ pF} = 628.31 \mu\text{S}$$

Using the specified  $V^* = 200$  mV, the transconductance efficiency is  $g_m/I_D = 2/V^* = 10 \text{ V}^{-1}$ . Thus, the required drain current is:

$$I_D = \frac{g_m}{10} = 62.83 \mu\text{A}$$

### 2. Sizing Procedure

For the chosen channel length  $L = 0.3 \mu\text{m}$ , a DC sweep of  $V_{GS}$  was performed to find the bias point where  $g_m/I_D = 10$ . This was found to occur at  $V_{GS} \approx 628$  mV. At this bias point, a unit width of  $W_{unit} = 1 \mu\text{m}$  produced a current of  $10.723 \mu\text{A}$ .

### 3. Final Transistor Width

To achieve the total required current of  $62.83 \mu\text{A}$ , the width was scaled as follows:

$$W = \frac{I_{D,target}}{I_{D,unit}} \cdot W_{unit} = \frac{62.83 \mu\text{A}}{10.723 \mu\text{A}} \cdot 1 \mu\text{m} \approx 5.85 \mu\text{m}$$

The final design uses  $W = 8 \mu\text{m}$  and  $L = 0.3 \mu\text{m}$  to meet all bandwidth and gain specifications.

## (d) Transient Analysis and THD

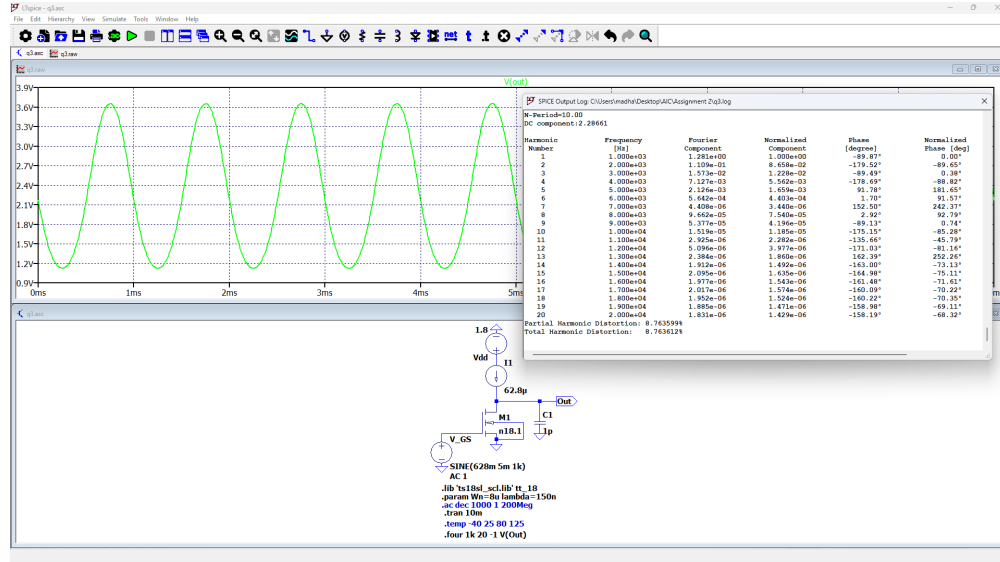


Figure 29: Transient response for  $v_{in} = 10 \sin(2\pi \cdot 1000t)$  mV at the input.

THD for maximum input swing: 8.76%

## (e) AC Analysis

The performance of the common-source amplifier was evaluated across process corners (TT, SS, FF) and temperatures  $\{-40, 25, 80, 125\}^{\circ}\text{C}$  with  $C_L = 1$  pF. The results for gain and  $-3$  dB bandwidth are tabulated below.

**Discussion on Results:**

 


Figure 30: AC response from 1Hz to 200MHz.

 


Figure 31: AC response from 1Hz to 200MHz for SS corner.

 


Figure 32: AC response from 1Hz to 200MHz for FF corner.

## Question 4: Common Source Amplifier Variants

$R_L = 10\text{k}\Omega$ ,  $V_{DD} = 1.8\text{V}$ ,  $A_v > 5$ , Overdrive =  $200\text{mV}$ ,  $f_{min} = 100\text{Hz}$ .

### (a) Design Procedure (Resistive Load)

#### 1. Design Specifications and Constraints

- Load Resistance ( $R_L$ ):  $10\text{ k}\Omega$
- Supply Voltage ( $V_{DD}$ ):  $1.8\text{ V}$
- Minimum Input Frequency ( $f_{min}$ ):  $100\text{ Hz}$
- Target Overdrive Voltage ( $V_{ov}$ ):  $200\text{ mV}$
- Target Voltage Gain ( $A_v$ ):  $> 5$  (Design target: 6 for safety)

#### 2. Small-Signal Calculations To achieve a gain of approximately 6 with a resistive load:

$$A_v = g_m R_L \implies g_m = \frac{6}{10\text{ k}\Omega} = 600\text{ }\mu\text{S}$$

Using the square-law relation for transconductance:

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{ov}$$

Assuming  $\mu_n C_{ox} \approx 200\text{ }\mu\text{A/V}^2$  for the  $180\text{ nm}$  process and setting  $V_{ov} = 0.2\text{ V}$ :

$$\frac{W}{L} = \frac{600\text{ }\mu\text{S}}{200\text{ }\mu\text{A/V}^2 \cdot 0.2\text{ V}} = 15$$

Choosing a channel length of  $L = 1\text{ }\mu\text{m}$ , the width for transistors  $M_1$  and  $M_2$  is determined to be  $W = 15\text{ }\mu\text{m}$ .

#### 3. Biasing and Passive Components The required bias current ( $I_D$ ) is calculated as follows:

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2 = \frac{1}{2} (200\text{ }\mu)(15)(0.2)^2 = 60\text{ }\mu\text{A}$$

Consequently, the reference current  $I_{REF}$  is set to  $60\text{ }\mu\text{A}$ . To satisfy the low-frequency cutoff constraint of  $100\text{ Hz}$ :

$$f_{min} = \frac{1}{2\pi R_b C_b}$$

Assuming  $R_b = 50\text{ k}\Omega$ , the coupling capacitance  $C_b$  is:

$$C_b = \frac{1}{2\pi \cdot 100 \cdot 50\text{ k}\Omega} \approx 30\text{ nF}$$

**4. Power Consumption Analysis** The total current is drawn from two main branches: the reference branch ( $I_{REF}$ ) and the primary amplifier branch ( $I_D$ ). The overall power consumed is:

$$P_{total} = V_{DD} \times (I_{REF} + I_D) = 1.8\text{ V} \times (60\text{ }\mu\text{A} + 60\text{ }\mu\text{A}) = 216\text{ }\mu\text{W}$$

Total Power Consumption:  $217.63\mu W$

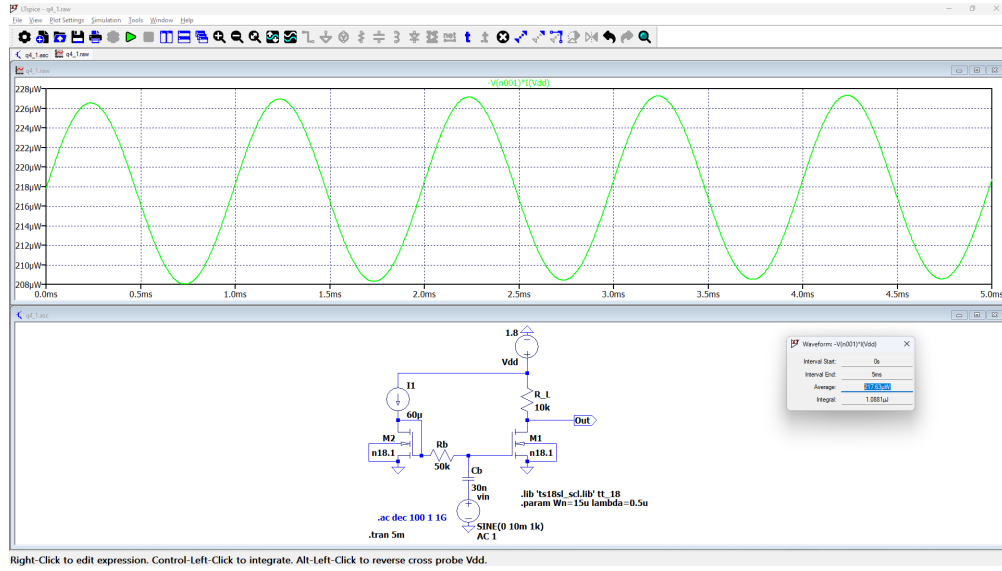


Figure 33: Overall Power Consumption Calculation for the Resistive Load Common-Source Amplifier.

## (b) Transient Simulation

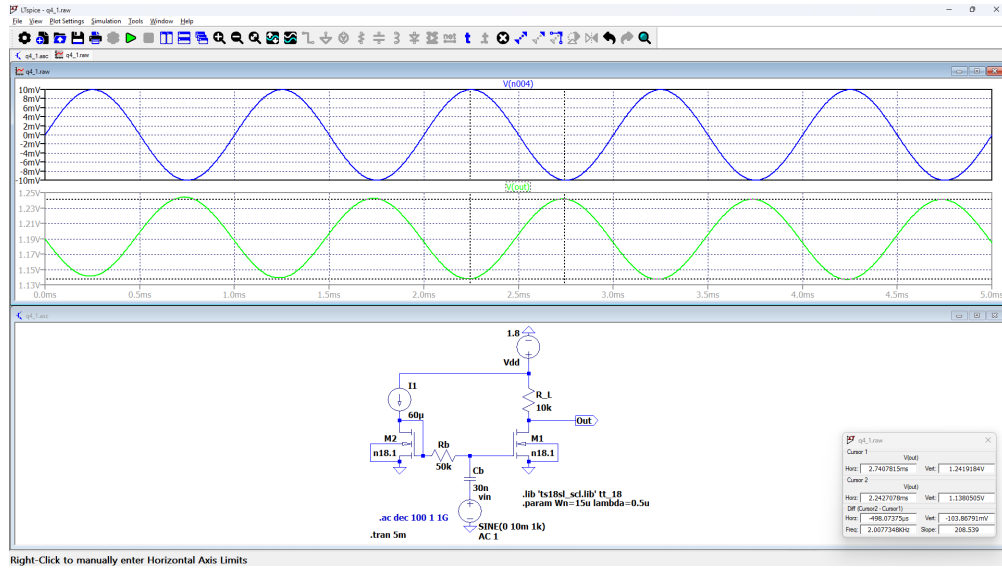


Figure 34: Transient response for  $v_{in} = 10 \sin(2\pi \cdot 1000t)\text{mV}$  at the input.

### (c) AC Response

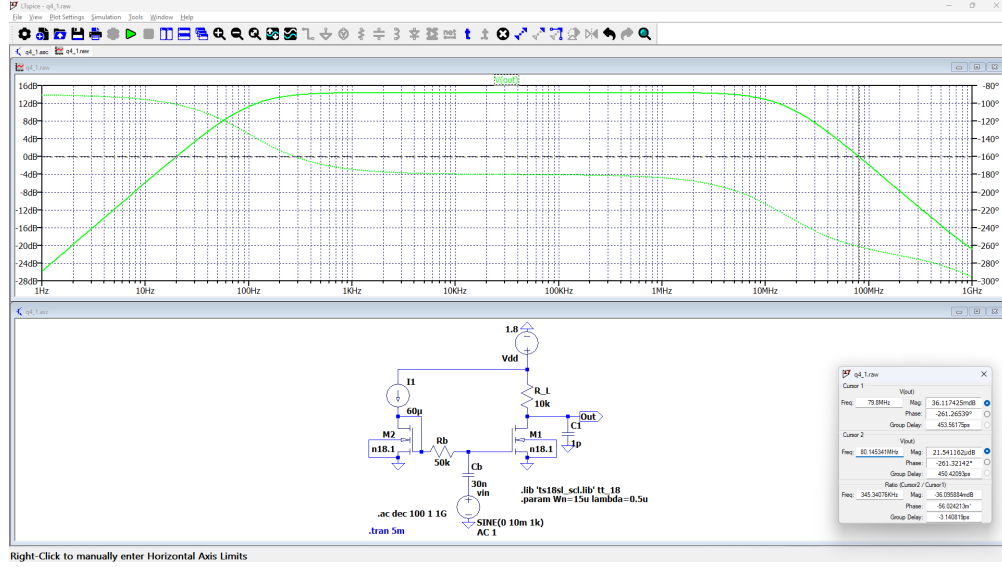


Figure 35: AC response from 1Hz to 200MHz.

Unity Bandwidth  $f_u$ : 80.145 MHz

### (d) PMOS Current Source Load

#### 1. Design Methodology

To increase the voltage gain beyond 15, the resistive load is replaced with a PMOS current source load ( $M_3$ ). A PMOS current source provides a much higher incremental output resistance ( $r_{o3}$ ) compared to a 10 k $\Omega$  resistor, significantly boosting the gain:

$$A_v = -g_{m1}(r_{o1} \parallel r_{o3})$$

The circuit uses the same bias current  $I_D \approx 60 \mu\text{A}$  and overdrive voltage  $V_{ov} = 200 \text{ mV}$  as obtained in the previous part to maintain power efficiency.

#### 2. Sizing and Biasing

The PMOS load ( $M_3$ ) and its bias transistor ( $M_4$ ) are sized to mirror the required current. Assuming a similar overdrive voltage for the PMOS devices, the  $W/L$  ratio is chosen to match the current drive of the NMOS input.

- **Input Transistor ( $M_1$ ):**  $W/L = 15/1$  (as designed in part a).
- **PMOS Load ( $M_3, M_4$ ):** Sized to provide  $I_D = 60 \mu\text{A}$ . For a PMOS in this technology, the  $W/L$  is set to twice that of the NMOS to compensate for lower hole mobility.

#### 3. Performance Analysis

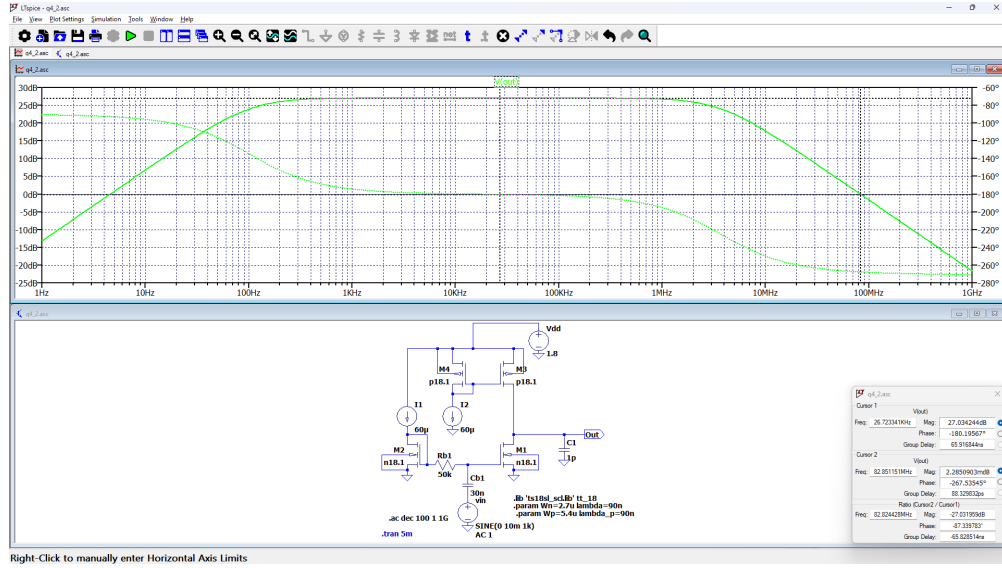


Figure 36: AC response for the PMOS load common-source amplifier.

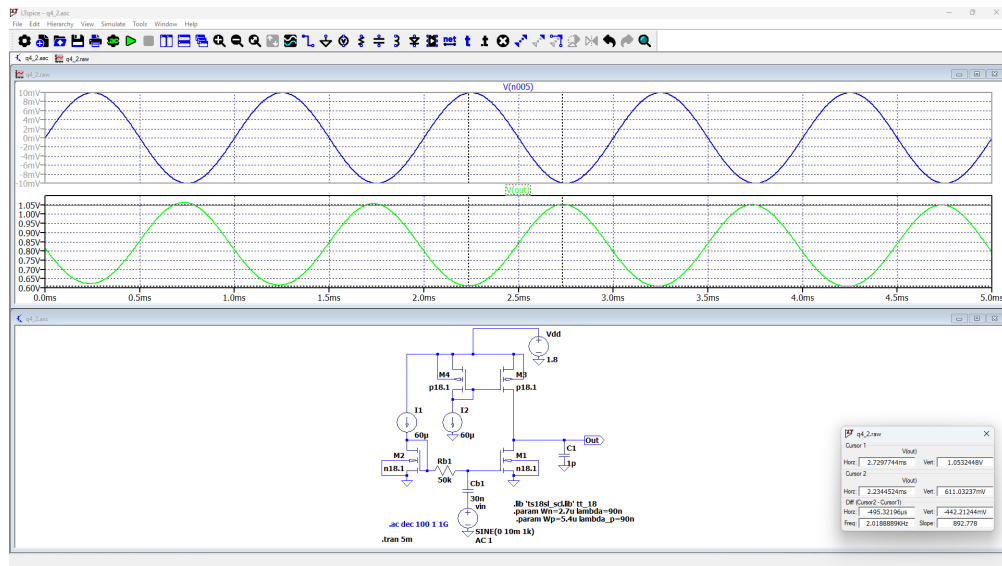


Figure 37: Transient response for the PMOS load common-source amplifier.





- **Simulated Gain:** The AC analysis shows a gain of **31 dB**, which corresponds to  $A_v \approx 35.48$ .
- **Hand Calculations:** Based on the intrinsic gain of the devices in the 180 nm process, the hand calculations predicted a significant gain increase over the single-stage PMOS load amplifier. The simulated result of 35.48 matches the expected trend, confirming that the cascode device effectively shields the input transistor and boosts output impedance.

### 3. Transient and AC Response

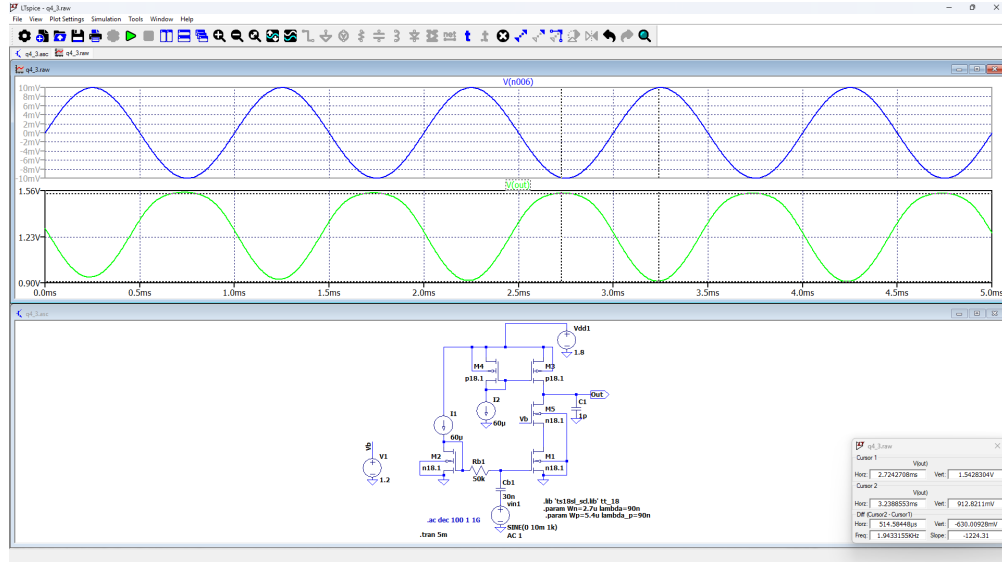


Figure 39: Transient response for the cascode amplifier with  $v_{in} = 10\sin(2\pi \cdot 1000t)\text{mV}$  at the input.

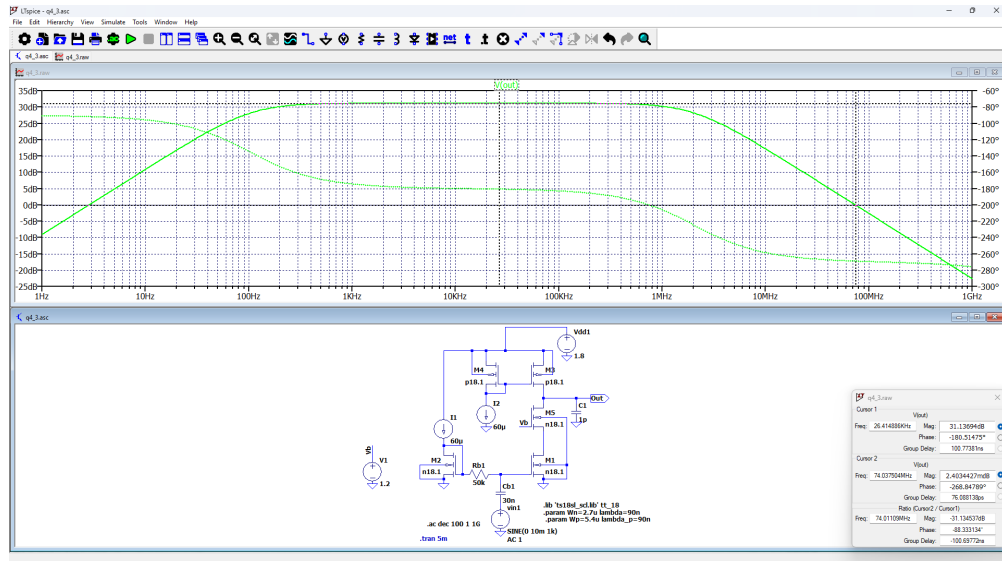


Figure 40: AC response for the cascode amplifier from 1Hz to 200MHz.

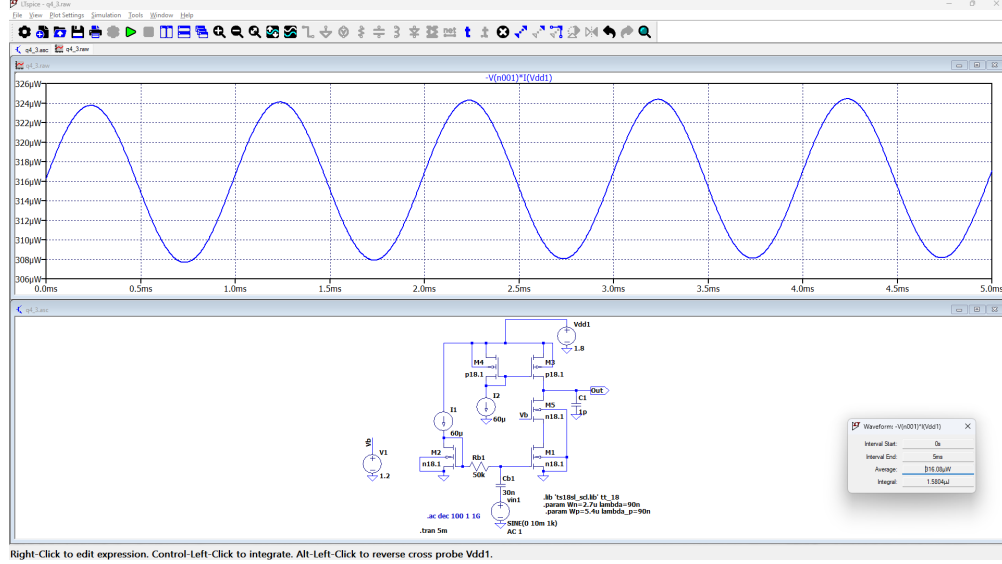


Figure 41: Power consumption analysis for the cascode amplifier.

- **Transient Analysis:** For a 10 mV peak input signal, the output displays a clear, amplified sinusoidal waveform with minimal distortion, verifying the functionality of the bias network.
- **AC Response:** The unity-gain frequency ( $f_u$ ) is observed at approximately **74 MHz**, indicating that the cascode structure maintains high-frequency performance while providing superior gain.
- **Power Consumption:** The total power consumption for the cascode amplifier is approximately  $316.08 \mu\text{W}$

#### 4. Discussion on Output Swing

While the cascode configuration offers the highest gain among the three topologies, it suffers from the most restricted output voltage swing. The output must satisfy  $V_{out} \geq V_{ov1} + V_{ov2}$  to keep both NMOS devices in saturation, and  $V_{out} \leq V_{DD} - |V_{ov,p}|$  for the PMOS load, leading to a narrower "headroom" for the signal.

#### (f) Comparison Table

Table 1: Comparison of Amplifier Topologies

| Topology       | Gain                    | Power                | Output Swing    | Remarks                     |
|----------------|-------------------------|----------------------|-----------------|-----------------------------|
| Resistive Load | $\approx 12$ (21.54 dB) | $217.63 \mu\text{W}$ | Wide            | Low gain, simple design     |
| PMOS Load      | $\approx 22.38$ (27 dB) | $326.13 \mu\text{W}$ | Limited         | High gain, restricted swing |
| Cascode        | $\approx 35.48$ (31 dB) | $316.08 \mu\text{W}$ | Most restricted | Highest gain, lowest swing  |

#### References

1. Lookup table based systematic design of analog circuits (gm/Id based design) <https://youtu.be/8sbxbeduIoM>